

GATE

1. What are the minimum number of 2-to-1 multiplexer required to generate a 2- input *AND* gate and a 2 - input *Ex - OR* ?
 - (a) 1 and 2
 - (b) 1 and 3
 - (c) 1 and 1
 - (d) 2 and 2